

## ECE 380: Prelab #9: Flip-flops and Counters

**Prelab tasks:** Before your lab session, you need to perform the following designs in Quartus Prime:

**Design A-1:** Design an edge-triggered D flip-flop in a .bdf file. The D flip-flop symbol is under c:/altera... > primitive > storage > dff, after you launch the Symbol dialogue window.

**Design A-2:** Design an edge-triggered D flip-flop using a VHDL code. Plot the outputs, Q and Q'.

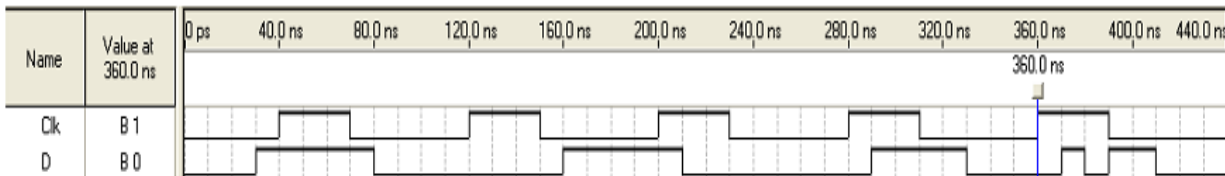


Fig. 1 Timing Waveforms for D-Flip Flop Inputs.

**Design B-1:** Design a JK flip-flop in a .bdf file. The JK flip-flop symbol is under c:/altera > primitive > storage > jkff, after you launch the Symbol dialogue window.

**Design B-2:** Design a JK flip-flop using a VHDL code. Plot outputs, Q and Q'.

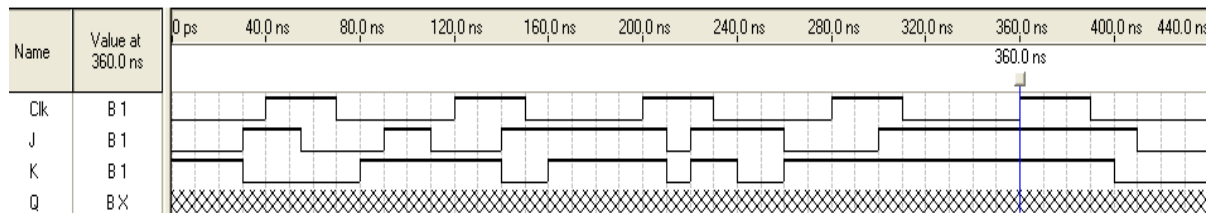


Fig. 2 Timing Waveforms for JK-Flip Flop Inputs.

**Design C-1 (BCD counter):** Use the VHDL code to create a BCD counter to count upward. This counter has the following control inputs: **En**,  **$\overline{reset}$** , **CLK**. The counting outputs are Q0, Q1, Q2, and Q3.

**$\overline{reset}$**  clears the outputs of the counter to 0. **En** enables the counting when **En**=1. When **En**=0, the counter stops. The counter sequentially counts from 0000, 0001, ..., to 1001, back to 0000, 0001, ..., to 1001, etc.

**Design C-2:** BCD counter with a LED display. Main procedures:

- Generate 1 Hz clock signal. Please follow Lab 2 Part II.
- Use your four-bit down-counter in Design C-1.
- Create a seven-segment LED display that shows 0 to 9.

- Connect 1 Hz clock signal with the four-bit counter. And use the seven-segment LED to display the counting numbers, 0 to 9.

<b><u>Pre-Lab (30%)</u></b>	<b>Score</b>	<b>TA initial</b>
30% Designs		

<b><u>Report (70%)</u></b>	
10% Introduction	
10% Procedures	
20% Results	
30% Conclusions	

<b><u>Lab Grade (100%)</u></b>	
<b><u>Bonus Points:</u></b>	