

ECE380: Pre-Lab #04: K-Maps

1. Given function $f(a,b,c,d) = \sum m(0, 2, 3, 8, 10, 11, 15)$, find its minimum SOP form using a K-Map.
2. Draw a logic diagram of the minimum SOP form of $f(a,b,c,d)$ using AND, NOT and OR gates.
3. Draw a logic diagram for the minimum SOP form of $f(a,b,c,d)$ using only NAND gates.
4. Given function $g(a,b,c,d) = \prod M(1, 4, 5, 6, 7, 9, 12, 13, 14)$, find its minimum POS form using a K-Map.
5. Draw a logic diagram of the minimum POS form of $g(a,b,c,d)$ using AND, NOT and OR gates.
6. Draw a logic diagram for the minimum POS form of $g(a,b,c,d)$ using only NOR gates.
7. Print out the table below for Lab #4. Do NOT fill in the blanks before the lab.

A	B	C	D	f	f min SOP	f NAND	g min POS	g NOR
0	0	0	0					
0	0	0	1					
0	0	1	0					
0	0	1	1					
0	1	0	0					
0	1	0	1					
0	1	1	0					
0	1	1	1					
1	0	0	0					
1	0	0	1					
1	0	1	0					
1	0	1	1					
1	1	0	0					
1	1	0	1					
1	1	1	0					
1	1	1	1					

<u>Pre-Lab (30%)</u>	Score	TA initial
15% K-maps		
15% Logic diagrams		

Lab Demo	TA Initials
f (min SOP)	
f (NAND)	
g (min POS)	
g (NOR)	

<u>Report (70%)</u>	
10% Introduction	
10% Procedures	
20% Results	
30% Conclusions	

<u>Final Lab Grade</u>	
-------------------------------	--