 


Lab 06: Design A

- Structural VHDL implementation of a 4-bit subtractor (ripple-carry structure)
 - Component: Full adder (one bits), which can be written in data-flow style
 - Instantiate the full adder four times and wire them (4 bits)
 - Make a 4-bit subtractor, using Full adders and NOT gates
 - Add an overflow flag (using XOR gate)
- You need to perform the following
 - Create a project, create VHDL codes, and compile
 - Create test vectors and perform functional simulation

4-bit subtractor

- Use four Full Adders and four NOT gates



Full adder in VHDL

- As in Lab 05

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY fulladd IS
    PORT ( Cin, x, y : IN STD_LOGIC ;
          s, Cout : OUT STD_LOGIC ) ;
END fulladd ;

ARCHITECTURE LogicFunc OF fulladd IS
BEGIN
    s <= x XOR y XOR Cin ;
    Cout <= (x AND y) OR (Cin AND x) OR (Cin AND y) ;
END LogicFunc ;
```

Ripple-carry adder in VHDL

- Structural style
- Declaration of Component
- Instantiation statement
- Named or positional association

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY adder4 IS
    PORT ( Cin : IN STD_LOGIC ;
          x3, x2, x1, x0      : IN STD_LOGIC ;
          y3, y2, y1, y0      : IN STD_LOGIC ;
          s3, s2, s1, s0      : OUT STD_LOGIC ;
          Cout                 : OUT STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL c1, c2, c3 : STD_LOGIC ;
    COMPONENT fulladd
        PORT ( Cin, x, y      : IN STD_LOGIC ;
              s, Cout         : OUT STD_LOGIC ) ;
    END COMPONENT ;
BEGIN
    stage0: fulladd PORT MAP ( Cin, x0, y0, s0, c1 ) ;
    stage1: fulladd PORT MAP ( c1, x1, y1, s1, c2 ) ;
    stage2: fulladd PORT MAP ( c2, x2, y2, s2, c3 ) ;
    stage3: fulladd PORT MAP (
        Cin => c3, Cout => Cout, x => x3, y => y3, s => s3 ) ;
END Structure ;
```

Ripple-carry adder in VHDL (cont'd)

- Data objective in vectors

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY adder4 IS
    PORT (    Cin    : IN    STD_LOGIC ;
             X, Y    : IN    STD_LOGIC_VECTOR(3 DOWNT0 0) ;
             S       : OUT   STD_LOGIC_VECTOR(3 DOWNT0 0) ;
             Cout    : OUT   STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL C : STD_LOGIC_VECTOR(1 TO 3) ;
    COMPONENT fulladd
        PORT ( Cin, x, y           : IN STD_LOGIC ;
              s, Cout             : OUT STD_LOGIC ) ;
    END COMPONENT
BEGIN
    stage0: fulladd PORT MAP ( Cin, X(0), Y(0), S(0), C(1) ) ;
    stage1: fulladd PORT MAP ( C(1), X(1), Y(1), S(1), C(2) ) ;
    stage2: fulladd PORT MAP ( C(2), X(2), Y(2), S(2), C(3) ) ;
    stage3: fulladd PORT MAP ( C(3), X(3), Y(3), S(3), Cout ) ;
END Structure ;
```

Lab 06: Design B

- Data-flow VHDL for the carry-lookahead 4-bit adder
 - Write down expressions for sum bits as well as carry-out bits
- You need to perform the following
 - Create a project, write your VHDL code, and compile
 - Perform functional simulation with test vectors
 - Use 7-segment LED display to show the results (in HEX format)
 - Download the design to DE1 board and test the DE1 board with test vectors

Design of CLA

- Carry-out bit:

- $c_1 = g_0 + p_0c_0$

- $c_2 = g_1 + p_1g_0 + p_1p_0c_0$

- $c_3 = g_2 + p_2g_1 + p_2p_1g_0 + p_2p_1p_0c_0$

- $c_4 = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0 + p_3p_2p_1p_0c_0$


- ...

- $c_n = g_{n-1} + p_{n-1}g_{n-2} + p_{n-1}p_{n-2}g_{n-3} + \dots + p_{n-1}p_{n-2} \dots p_2p_1g_0 + p_{n-1}p_{n-2} \dots p_2p_1p_0c_0$

- Sum bit still: $s_{n-1} = c_{n-1} \oplus x_{n-1} \oplus y_{n-1}$

Structure of CLA

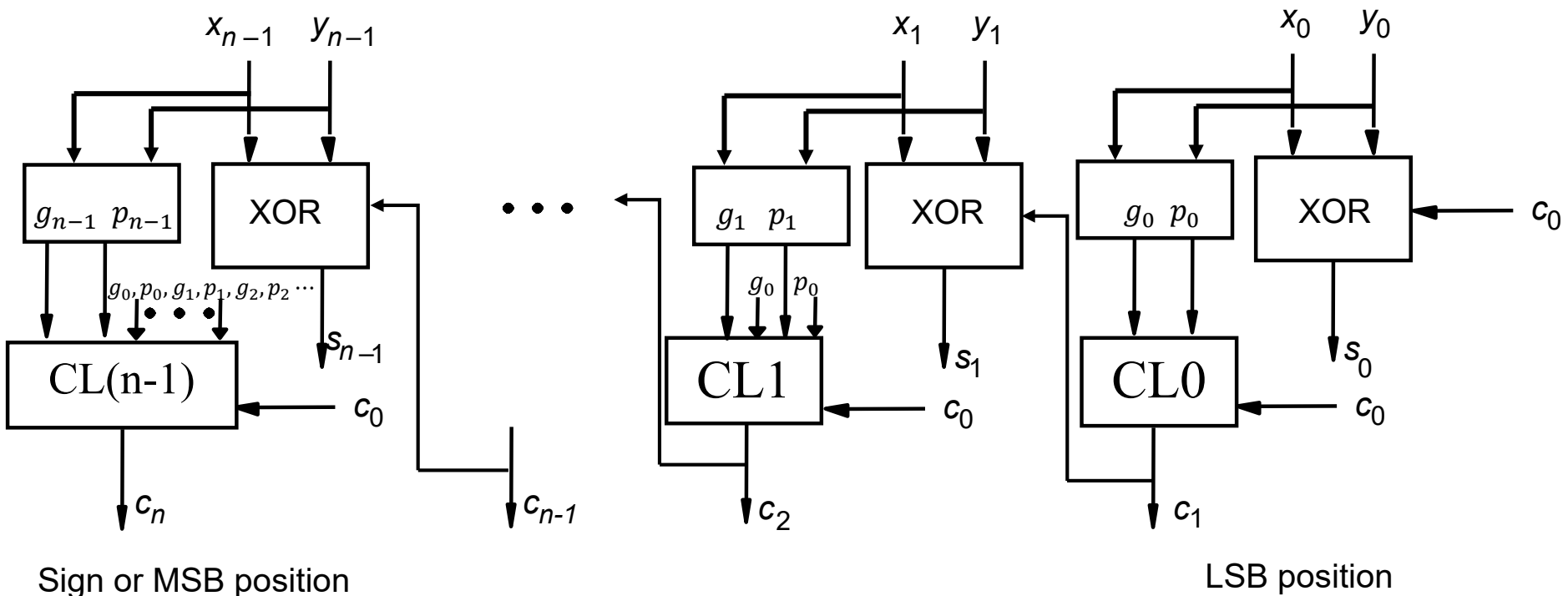- No full adders
- CL=Carry-lookahead has inputs
 - c_0, g_0, p_0 for c_1 (stage 0)
 - c_0, g_0, p_0, g_1, p_1 for c_2 (stage 1)
 - $c_0, g_0, p_0, g_1, p_1, g_2, p_2$ for c_3 (stage 2)
 - And so on



Further explanation

- Generate input/output lists:
 - Input list should contain 1) vectors X , Y as data inputs, both 4-bit wide and 2) a carry-in, $c0$.
 - Output list should contain 1) sum vector S , 4-bit wide and 2) a carry-out, $Cout$.
- Specify the input/output relationship.
 - Establish multiple internal signals, $c1$, $c2$, $c3$, $c4$, which are the carry-out signals for each stage of the adder. See page 12, for equations of these internal signals.
 - Write the sum bits, $S[0]$ to $S[3]$, in terms of inputs, X , Y , and internal carry-out. See page 12 for equations
 - Finally $Cout=c4$.